Chocolate Vending Machine

Submitted by: Group 85

Group members:

Tejas Musale(2019A3PS0409G)
Aarohi Khodkumbhe(2019A3PS0451G)
Harsh Nagle(2019A3PS0336G)
Saarth Jhaveri(2019A8PS0669G)
Atharva Karandikar(2019A7PS0083G)
Muhammad Aatiq(2019AAPS0192G)

Date: - 19.04.2021

f20190409@goa.bits-pilani.ac.in f20190451@goa.bits-pilani.ac.in f20190336@goa.bits-pilani.ac.in f20190669@goa.bits-pilani.ac.in f20190083@goa.bits-pilani.ac.in f20190192@goa.bits-pilani.ac.in

Problem statement

This automatic machine vends three different types of chocolates.

Perk: Rs. 5.00 Five-Star: Rs10 Dairy Milk: Rs20.

The currency has to be given in terms of 5 Rupee coins. A weight sensor is used to detect whether the coin is a Rs 5 coin or not. There are three buttons available for the selection of the chocolate. After the chocolate has been selected the user has to put the correct currency into the coin slot. When the user has dropped the entire amount into the slot, the machine dispenses the correct chocolate. LED's are used as indicators to show if any of the chocolates being vended are not available.

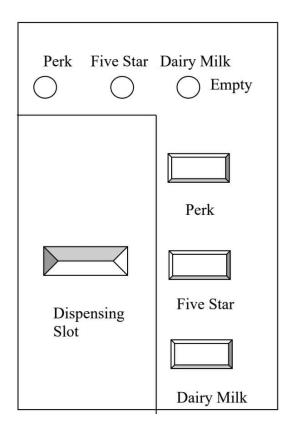


Table of Contents:

User Requirements	4
Technical Specifications	4
Assumptions	5
Justifications	5
Components used with Justification	6
Address Map	8
Flow Chart – Main Program	10
Flow Chart – ISR	12
Variation in Proteus Implementation with justification:	13
Firmware	14
List of Attachments	15

User Requirements

- 1. The system is a vending machine that gives chocolate of three types i.e., Dairymilk, Perk, 5Star.
- 2. The prices of the chocolates are as follows:
- Dairy Milk- Rs.20
- 5Star- Rs.10
- Perk- Rs.5
- 3. The user presses the button for chocolate selection and then puts in money (currency in terms of 5 Rupee coin only).

Technical Specifications

- 3 LEDs are used to indicate if chocolate is available in the machine. Each LED is 5 Volt.
- 2. The motor is used to dispense the correct chocolate.
- 3. A pressure sensor (with a conversion factor of 1KPa = 20 mV) is used to sense the pressure of the input coin.
- 4. Analog To Digital Converter is used to digitize the reading taken by a pressure sensor. The resolution of the ADC is 5V/255 = 19.607mV≅20mV
- 5. A unipolar Stepper Motor is used to serve the purpose of the dispensing slot.

Assumptions

- 1. User can only press one key at a time:
 - Perk
 - 5 Star
 - Dairy Milk
- 2. Users can put at most 4 coins, over 4 coins is considered invalid.
- 3. User puts in the coin one by one, after every 10 sec.
- 4. Users can put only Rs.5 coins as no other denominations are considered valid.
- 5. A maximum of 100 Dairy Milk, Perk, and 5star are available.
- 6. In each transaction, the user can only get one chocolate of a particular type.
- 7. The pressure of a Rs.5 coin is 1KPa which gives a 20 mV voltage.

Justifications

None.

Components used with Justification

- 8086
- 8284
- ADC 0808 → Single Analog input.
- 8255(1) → To Interface ADC, 3 input switches (used for selecting the chocolate) and 3 LED's (which glow when a chocolate is unavailable).
- <u>8255(2)</u> →To Interface the stepper motor (used to dispense the required chocolate or invalid number of coins).
- 8254 → To generate an ADC clock of 1Mhz from the 5Mhz clock available and to generate the 10s interrupt (time given to the user to place a coin).
- 8259 →Interrupt of 10s given from the timer.
- 2716 → 4 nos. The smallest ROM chip available is 2K and as we need to have even and an odd bank and ROM is required at reset address which is at FFF0H and 00000H - where there is the IVT.
- LS138 → 2 decoders (one for memory decoding and one for the decoding of the ports), LS373 and LS245.
- <u>Stepper motor</u> → Used to dispense chocolates.
- 6116 → 2 nos. Smallest RAM chip available is 2 K and we need an odd and even bank. We need RAM for stack and temporary storage of data.

Sequence1	1	0	1	0
Sequence2	1	0	0	1
Sequence3	0	1	0	1
Sequence4	0	1	1	0
Sequence5	1	0	1	0

- MPX4250, pressure sensor specifications
 → MPX4250 is a silicon
 pressure sensor designed for a wide range of applications, particularly to
 interface with microcontroller or microprocessor with A/D inputs.
- 1. Pressure range 0-250KPa
- 2. Voltage input(DC supply to the pressure sensor)-4.85-5.35V
- 3. Typical Voltage- 5.1V
- 4. Resolution($\Delta V/\Delta P$) \cong 20 mv/KPa
- 5. 6 pins input (3 pins are left unused).

Pin	Signal	Input/Output	Description
1	Vout	Output	Voltage output of the pressure sensed
2	GND	Input	Ground
3	Vcc	Input	Typical voltage supply given to excite the pressure sensor.

Address Map

Memory Map (Both RAM and ROM chips used are 2K)

 $ROM1 \rightarrow 00000H - 00FFFH$ (Even Bank begins at 00000H and ends at 00FFEH and Odd Bank begins at 00001H and ends at 00FFFH)

RAM1→ 01000H – 01FFFH (Even Bank begins at 01000H and ends at 01FFEH and Odd Bank begins at 01001H and ends at 01FFFH)

ROM2→ FF000H – FFFFFH (Even Bank begins at FF000H and ends at FFFFEH and Odd Bank begins at FF001H and ends at FFFFFH)

<u>I/O Map</u>

8255(1)→ 0000 - 0006H (PortA-00H, PortB-02H, PortC-04H, Creg-06H)

8255(2)→ 0008 - 000EH (PortA-08H, PortB-0AH, PortC-0CH, Creg-0EH)

8254→ 0010 - 0016H (Counter0-10H, Counter1-12H, Counter2-14H, Creg-16H)

8259→ 0018 - 001AH

Interrupt 40H is used in the program. Therefore, IP= 00100H (40*4).


<u>IVT-</u>


IP	t_isr
CS	0000Н

DESIGN


Separate pdf attached- hardware_design.pdf

Flow Chart – Main Program

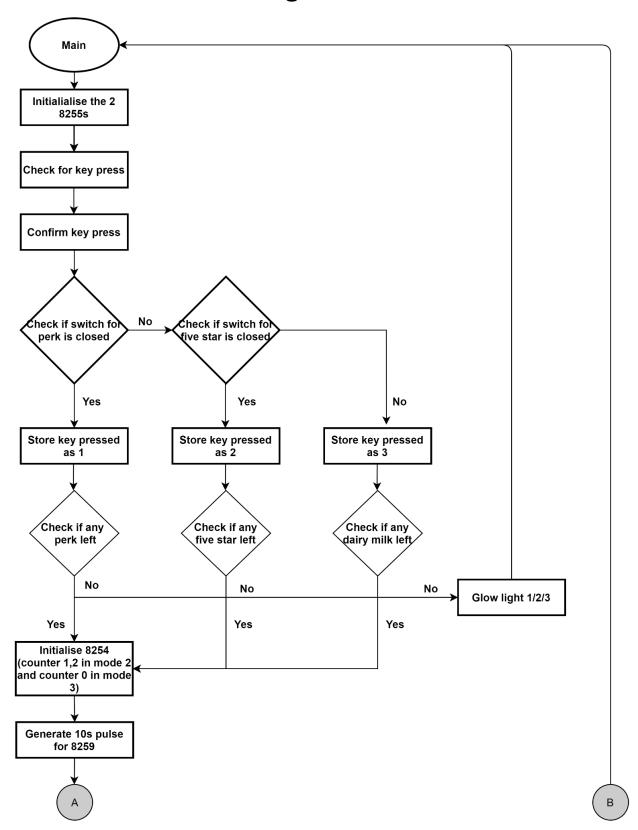

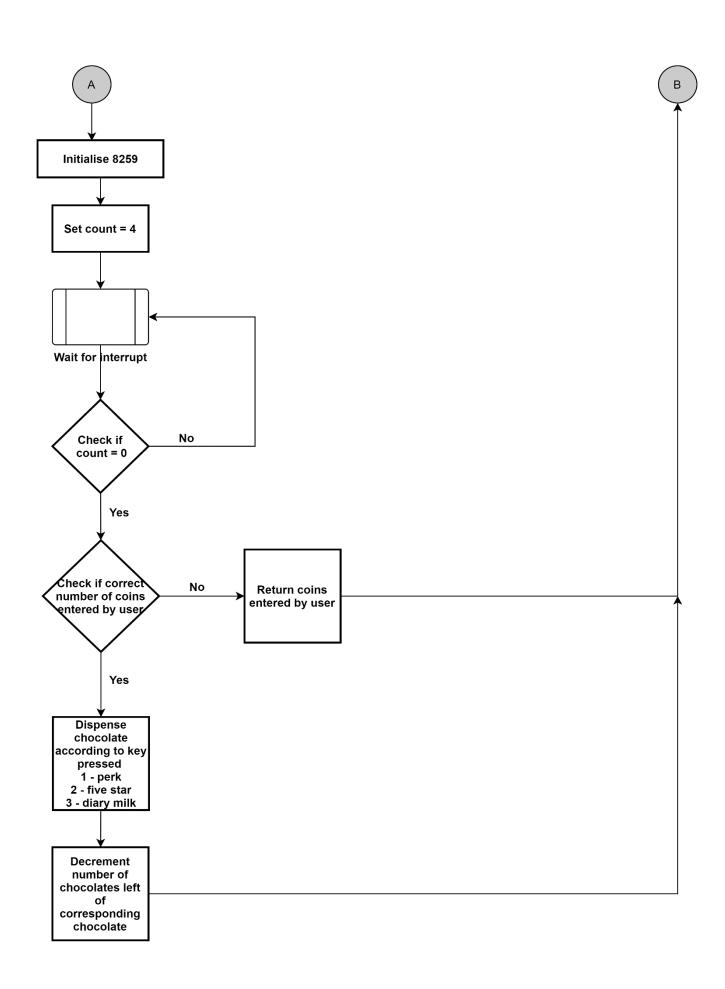

Flow Chart - ISR

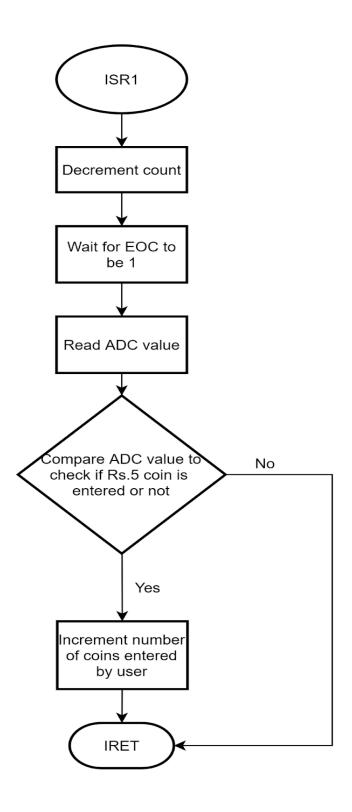

Variation in Proteus Implementation with justification:

- 1. Using 10s delay as 8259 does not work in proteus and the Timer Int replaced by software delay as 10s.
- 2. ROM in only 00000 as proteus allows to change reset address.
- 3. Using 8253 as 8254 not available in Proteus.
- 4. 2732 is used as 2716 not available in Proteus.
- 5. Using a gate-based circuit for memory does the same as LS 138 here.
- 6. 8259 not there justification is as per point 1.

Firmware

Implementation using emu8086 attached - design2.asm

List of Attachments

- 1. Complete Hardware real design hardware_design.pdf
- 2. Manuals
 - a. ADC
 - b. 8086
 - c. 8255
 - d. 8259
 - e. 8253
 - f. NEMA 17 (Stepper motor)
 - g. MPX4250 (Integrated silicon pressure sensor)
- 3. Proteus File final_design.dsn
- 4. EMU 8086 ASM File design2.asm
- 5. Binary file after assembly **design.bin**

THANK YOU!